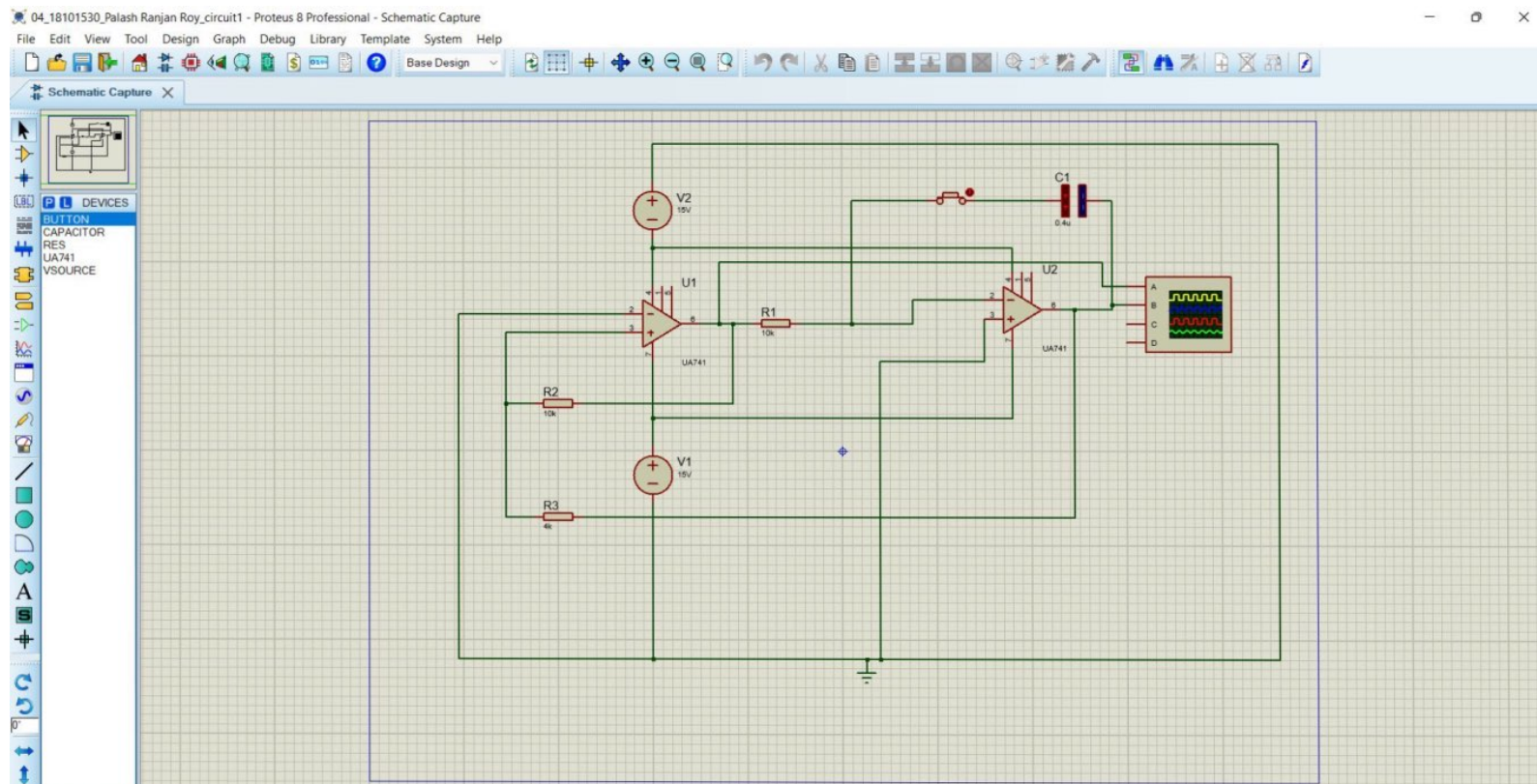



Palash Ranjan Roy

ID-18101530

Sec-04


Lab ~~05~~ 06



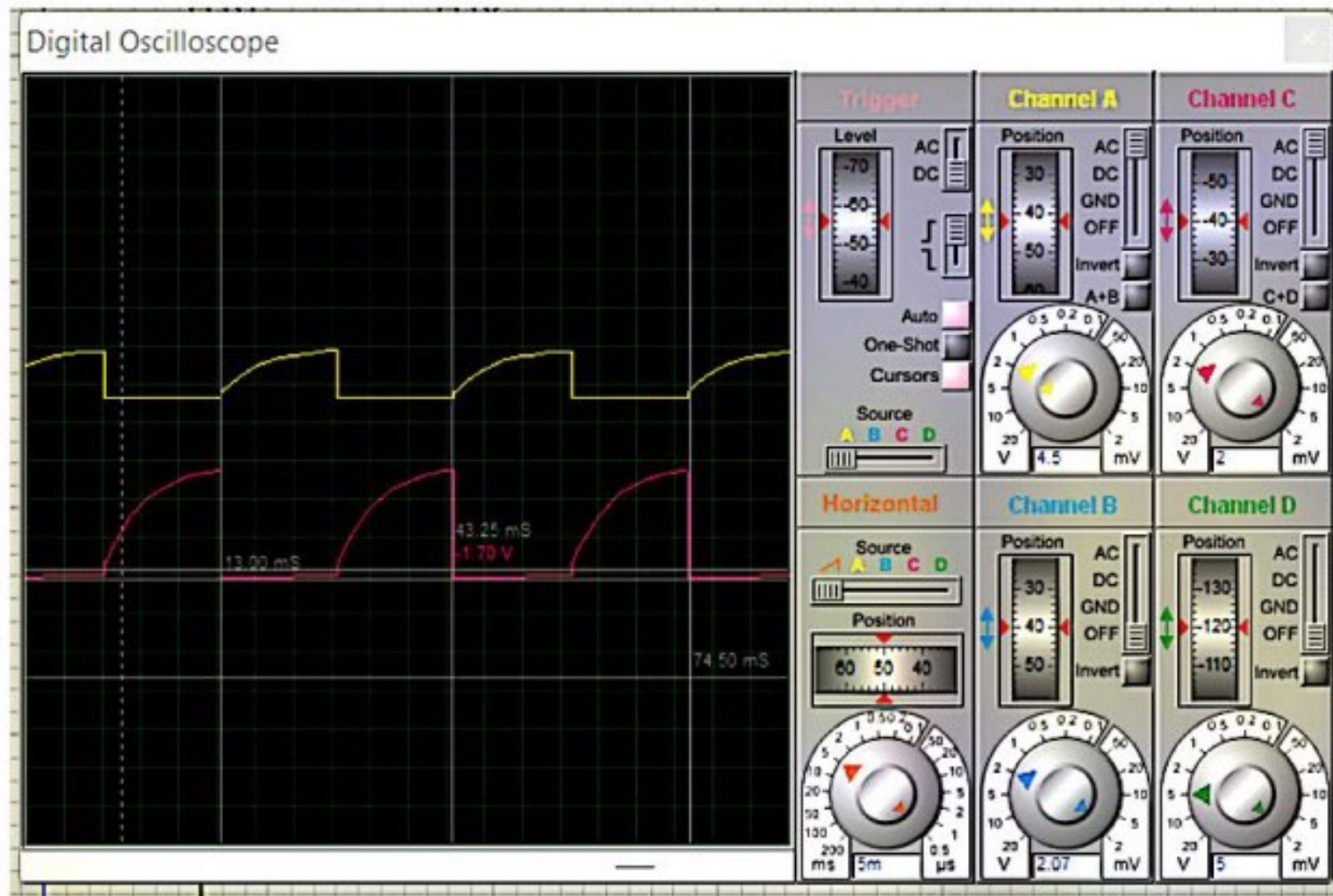

Report:

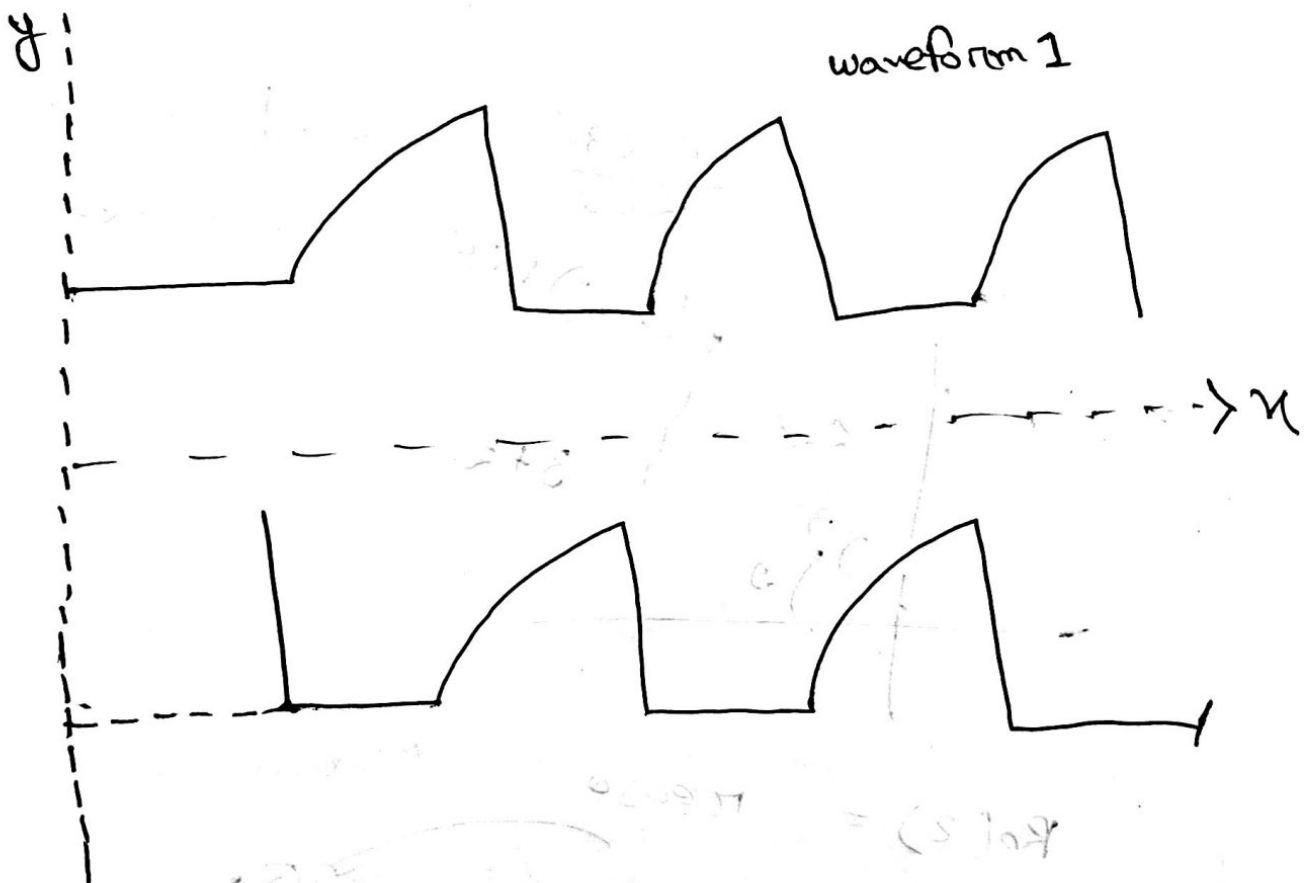1. The output waveforms achieved from protius simulation:



2. There is slight deviation in the experimental output wave shape from the desired wave.

In real life there is some system loss and the capacitor take some time to charge and discharge. There is also internal hidden resistance. That is why time period increased by $T = RC$

3. $R_1 = R_4 = 1 \text{ K}\Omega$; $R_2 = R_3 = 4.7 \text{ K}\Omega$
 $C_1 = C_2 = 4.7 \mu\text{F}$

Theoretical Calculation:

$$t_1 = 0.69 \times R_1 R_3$$

$$= 0.69 \times (4.7 \times 10^6) \times (4.7 \times 10^3)$$

$$= 0.0152421 \text{ s}$$

$$t_2 = 0.69 \times C_2 R_2$$

$$= 0.69 \times 4.7 \times 10^{-6} \times 4.7 \times 10^3$$

$$= 0.0152421 \text{ s}$$

Total period, $T = t_1 + t_2$

$$= 30.4842 \text{ ms}$$


From simulation

$$T = T_2 - T_1 = (.43.25 - .13.00)$$

$$= \cancel{.30.25} = 30.25 \text{ ms}$$

The experimental value and the theoretical value is quite similar. The difference is, $(\cancel{.30.48} - \cancel{.30.25}) = \cancel{0.23} \text{ ms}$ which is negligible.

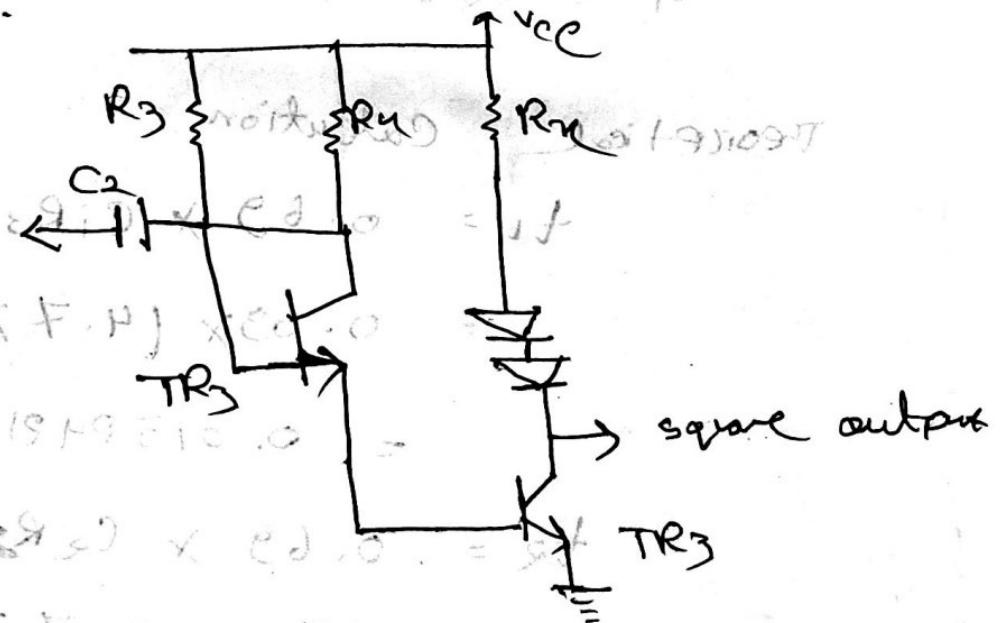4. It is possible to use the multivibrator to create variable frequency square wave generator.



Here, TR2 and TR3 is dependent on each other. So, when TR2 is off TR3 will be turned off as well. On the other hand, when TR2 is on TR3 will be turned on.

5. In astable multivibrator a variable resistor can be used to regulate the duty cycle of the circuit.

$$\text{duty cycle} = (R_1 + R_2) / (R_1 \times R_2)$$

A variable resistor is used to adjust the duty cycle of the PWM produced by the PWM generator. So here if we change R_1 and R_2 's values the goal can be achieved.